

S.Y. Diploma : Sem. III  
[EJ/EN/ET/EX/EV/ED/IU/DE/IS/IC/IE/MU]  
**Electronics Devices and Circuits**



Time: 3 Hrs.]

Prelim Question Paper


[Marks : 100

- Instructions :**
- (1) All questions are compulsory.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data if necessary.
  - (5) Preferably, write the answers in sequential order.

1. (a) Attempt any **SIX** of the following : [12]
- (i) What are transistor biasing circuits and name the different biasing circuits?
  - (ii) Draw Drain (Output) characteristics of N-channel JFET & show different regions of operation on it.
  - (iii) Define multi-stage amplifier and state its necessity.
  - (iv) Define intrinsic standoff ratio ( $\eta$ ) of UJT.
  - (v) Give the symbol of UJT and state why it is called uni-junction transistor.
  - (vi) State Barkhausen criterion on oscillation.
  - (vii) State the two types of transistor and give their symbols.
- (b) Attempt any **TWO** of the following : [8]
- (i) Give the comparison between -ve feedback and +ve feedback.
  - (ii) Explain self-bias circuit used in JFET.
  - (iii) Draw input characteristics for N-P-N transistor in common-Base configuration & explains it.
2. Attempt any **FOUR** of the following : [16]
- (a) Draw block diagram of voltage amplifier. Show important parameters of amplifier on it and state the requirements of good voltage amplifier.
  - (b) Give the comparison between 3 configurations of transistor.
  - (c) Draw the functional block diagram of controlled series voltage regulator and explain the functions of each block.
  - (d) State the types of -ve feedback amplifiers and draw their functional block diagrams. Also state the effect on  $R_{IN}$  and  $R_O$ .
  - (e) Draw UJT relaxation oscillator circuit and explain its working with the help of 3 waveforms.
  - (f) Draw the circuit diagram of direct coupled amplifier and explain its working.
3. Attempt any **FOUR** of the following : [16]
- (a) Give comparison between voltage amplifier and power amplifier.
  - (b) Write a note on "Thermal run-away" in transistor. Why is showed be avoided.
  - (c) Draw the block diagram of multi-stage amplifier and derive an expression for its overall voltage gain.
  - (d) Define the following characteristics of regulated power supply : (i) Voltage regulation or Load regulation, (ii) Line regulation, (iii) Ripple rejection and (iv) Output impedance.
  - (e) Define sweep speed for a sweep waveform. Name and define the errors which are present in sweep signal.

(f) A feedback amplifier is shown in figure calculate :

- (i) Value of feedback factor
- (ii) Voltage gain  $A$  of amplifier without feedback
- (iii) The feedback voltage  $V_f$ .

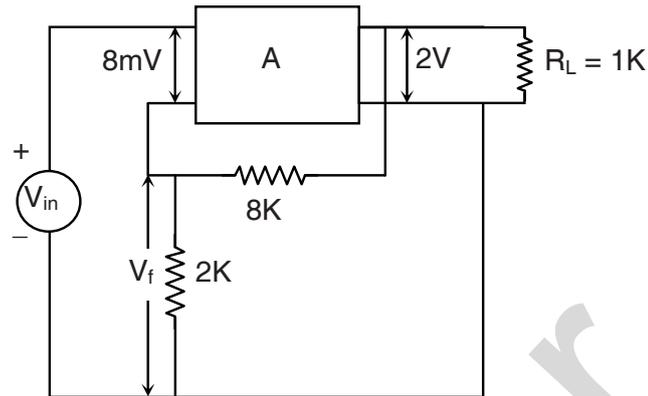

4. Attempt any **FOUR** of the following :

[16]

- (a) Draw the circuit diagram of Class B push-pull amplifier and explain its working.
- (b) Give the comparison between BJT and JFET.
- (c) Write a note on cross-over distortion.
- (d) Find 'f' for UJT relaxation oscillator if  $R = 10k$ ,  $C = 0.1\mu F$ . Assume suitable value for  $\eta$ .
- (e) Prove that reverse leakage current in common emitter is 100 times more than the reverse leakage current of common base configuration. i.e. prove that  $I_{CEO} = 100 I_{CBO}$ .
- (f) Explain the working of RC phase shift oscillator.

5. Attempt any **FOUR** of the following :

[16]

- (a) Explain why stability of the amplifies improves when  $-ve$  feedback is used.
- (b) Give the comparison between series and parallel resonant circuit.
- (c) Draw the circuit diagram of single ended or transformer coupled class A amplifier and explain its working.
- (d) State the advantages and disadvantages of  $-ve$  feedback amplifier.
- (e) Derive an expression for the closed loop gain of  $-ve$  feedback amplifier.
- (f) Draw functional block diagram of I.C. 723 and explain it.

6. Attempt any **FOUR** of the following :

[16]

- (a) Draw the circuit diagram of Zener diode voltage regulator and explain its working.
- (b) Draw the circuit diagram of 2 stage transformer coupled amplifier and explain its working.
- (c) Define voltage gain ( $A_V$ ), current gain ( $A_I$ ) and power gain ( $A_P$ ) of the amplifier and derive the relation between them.
- (d) Draw the circuit diagram of single tuned voltage amplifier and explain its working with the help of frequency characteristics.
- (e) Give the advantages and dis-advantage of Class B push-pull power amplifier.
- (f) Give comparison of class A, B and C power amplifier.

