

Basic Electronics & Mechatronics

Time: 3 Hrs.]

Prelim Question Paper

[Marks : 100

- Instructions :**
- (1) All questions are compulsory.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data if necessary.
 - (5) Preferably, write the answers in sequential order.

1. (a) Attempt any **SIX** of the following : [12]
- (i) What is extrinsic Semiconductor?
 - (ii) Draw the symbols of LED?
 - (iii) Draw the symbols of BJT (nnp and pnp)
 - (iv) List types of coupling used in Multistage Amplifier.
 - (v) List any four application of OP-Amp.
 - (vi) List application of Dual timer IC '556'.
 - (vii) Explain in brief with neat sketches : Fan in.
 - (viii) Enlist advantages of LVDT.
- (b) Attempt any **TWO** of the following : [8]
- (i) Draw and explain Energy level diagram of semiconductor and insulator.
 - (ii) Explain the operation of PN junction under reverse bias condition.
 - (iii) Explain construction and working principle of zener diode.
2. Attempt any **FOUR** of the following : [16]
- (a) Describe V-I characteristics of point contact diode, with application.
 - (b) Draw the circuit diagram of a half wave rectifier. Draw its input-output waveforms.
 - (c) Define the following forms :
 - (i) Peak inverse voltage.
 - (ii) Ripple factor
 - (iii) Rectification efficiency
 - (iv) Transformer utilization factor (TUF)
 - (d) Explain the principle of operation of capacitor input (or π filter) with advantages and disadvantages.
 - (e) With a neat diagram. Explain the working of NPN transistor.
3. Attempt any **FOUR** of the following : [16]
- (a) Given $\beta = 150$, $i_B = 15\mu A$ and transistor is biased in the forward active mode to find $i_C = ?$, $i_E = ?$ and $\alpha = ?$

- (b) Explain common Emitter configuration with the help of input and output characteristics.
- (c) Explain need of cascade Amplifier and coupling used in Amplifiers.
- (d) "Explain two stage impedance coupled CE amplifier with neat sketch"
- (e) Compare to different types of coupling on the basis of following factor :
 - (i) Cost
 - (ii) Space and weight
 - (iii) Frequency response
 - (iv) Impedance matching
 - (v) Distortion
 - (vi) Hum
 - (vii) Voltage gain
 - (viii) Application

4. Attempt any **FOUR** of the following : [16]

- (a) Define the following parameters of 'OP-amp'
 - (i) Input bias current (I_B)
 - (ii) Input offset current (I_{ios})
 - (iii) Open Loop voltage gain.
 - (iv) Differential input resistance (R_i)
- (b) Determine S.R. of a OP-amp at room temp. which has unity cross-over frequency of 5MHz.
- (c) Explain with symbol inverting and Non-inverting Amplifier.
- (d) Explain summing scaling and averaging amplifier?
- (e) Explain process of instrumentation amplifier with any four requirement of instrumentation amplifier.

5. Attempt any **FOUR** of the following : [16]

- (a) With neat block diagram explain operation of Time ic 555.
- (b) Give the symbol, truth table and function for the following gates.
 - (i) NOT
 - (ii) OR
 - (iii) AND
 - (iv) NOR
- (c) Prove the following logic expression using Boolean algebra.
$$AB + CD = (A + C)(A + D)(B + C)(B + D)$$
- (d) Design AND using NOR gate.
- (e) Design a Half adder, using K-map.

6. Attempt any **FOUR** of the following : [16]

- (a) Define transducer & classified on the basic of active type and passive type.
- (b) Explain with block diagram "AC signal conditioning system".
- (c) Describe "AC tachogenerator".
- (d) Explain procedure of "LVDT" with neat sketch.
- (e) Explain with neat sketch. "Rotameter".

