

S.Y. Diploma : Sem. III
[DE/EJ/ET/EN/EX/IE/IS/IC]
Electric Circuits and Networks
Prelim Question Paper Solution



Time: 3 Hrs.]

[Marks : 70

- Instructions :**
- (1) All questions are compulsory.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data if necessary.
 - (5) Preferably, write the answers in sequential order.

1. Attempt any **FIVE** of the following : [10]


- (a) What is Power factor and its significance?
- (b) Write a equation of impedance R_L and R_C circuit.
- (c) Draw power triangle for series circuit.
- (d) Three resistances of 3Ω each are connected in star find equivalent resistance when connected in delta.
- (e) What are the advantage and disadvantages of Superposition theorem?
- (f) Write the equation of Open circuit Z parameters.

2. Attempt any **THREE** of the following : [12]

- (a) Draw voltage triangle, power triangle, impedance triangle of series RC circuit.
- (b) State and explain the Norton's theorem.
- (c) What do you mean by redundant sources?
- (d) Define impedance. What is its unit? State the factors on which it depends.

3. Attempt any **THREE** of the following : [12]

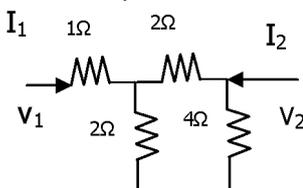
- (a) A 50 Hz voltage of 230 volt rms value is applied across a capacitor of $26.5 \mu\text{F}$. Calculate :
 - (i) The capacitive reactance
 - (ii) Write the time equation for voltage and the resulting current. Let the zero axis of the voltage be at $t = 0$
- (b) Find the z parameters for the network shown in Figure.




- (c) Prove that $\omega_0 = \sqrt{\omega_1 \omega_2}$.
- (d) How to convert from Pi to T and vice versa?

4. Attempt any **THREE** of the following : [12]

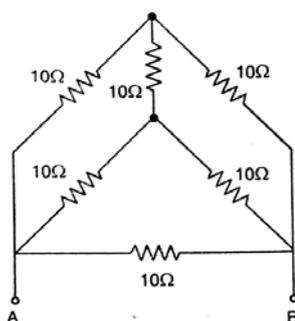- (a) A choke coil takes a current of 2.5 Amp when connected across 250 V, 50 Hz a.c. supply and consumes 400 Watts. Calculate :
 - (i) Power factor
 - (ii) Resistance of coil
 - (iii) Inductance of coil
- (b) Calculate equivalent resistance R_{AB} using delta star transformation (Refer figure).




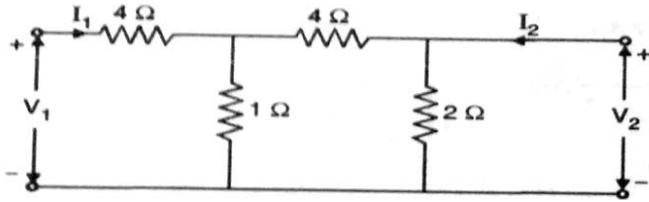(c) Obtain ABCD parameters for the network shown in figure.



(d) $v = 150 \sin(314t)$ and $i = 10 \sin\left(314 + \frac{\pi}{4}\right)$. Find circuit component connected in series.

(e) Determine the current in 2Ω resistance in figure using Mesh analysis.

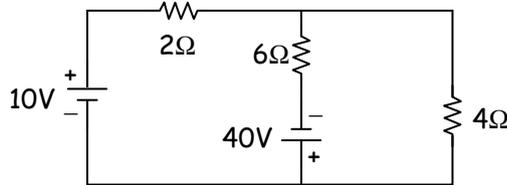


5. Attempt any **TWO** of the following :

[12]

(a) A coil having resistance of 5Ω and inductance of 0.2 H is arranged in parallel with another coil having resistance of 1Ω and inductance of 0.08 H . Calculate the current through the combination and power absorbed when a voltage of 100 V , 50 Hz is applied. Use impedance method.

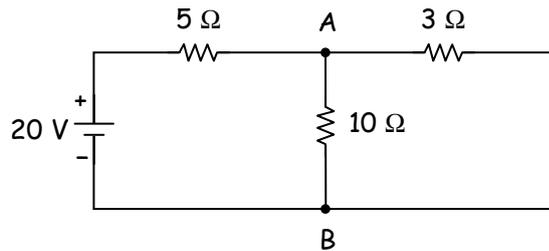(b) Calculate the current in 10Ω resistance using Norton's theorem shown in figure.



(c) A coil of resistance 15Ω and inductance of 0.05 H connected in series with $100\mu\text{F}$ capacitor across 230 V , 50 Hz ac supply find :

- (i) Current
- (ii) Power factor of circuit
- (iii) Voltage drop across coil
- (iv) Voltage across capacitor


6. Attempt any **TWO** of the following :

[12]

(a) A series circuit has the following characteristics $R = 10\Omega$, $L = \frac{100}{\pi}\text{ mH}$, $C = \frac{500}{\pi}\mu\text{F}$.


- Find : (i) The current flowing when the applied voltage is 100 V at 50 Hz .
- (ii) The power factor of the circuit
- (iii) What value of supply frequency would produce series resonance?

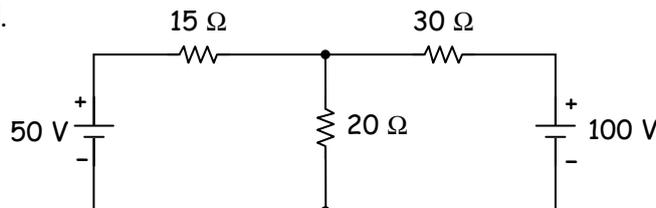(b) Determine the current through 20 ohm resistance in figure using node analysis method.



(c) For a circuit shown in figure. Find :

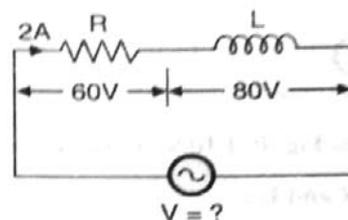- (i) Values of R and L
- (ii) Total voltage
- (iii) Impedance
- (iv) Power factor



□ □ □ □ □

S.Y. Diploma Sem-III: Paper Discussion Schedule

Branches	Date	Day	Timing	Centres
Electronics Group	8 Nov. 2018	Thursday	9 a.m. to 11 a.m.	Dadar